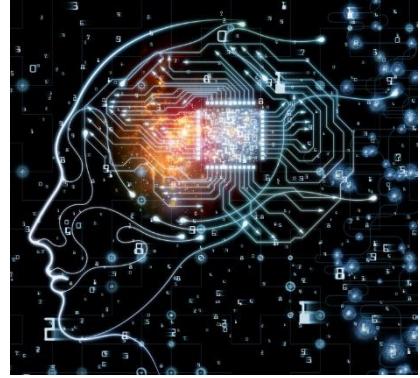


Logic Gates



Digital Logic and Design



ArfanShahzadTech



WhatsApp-Contact Us
0345-5922495

Arfan Shahzad
arfanskp@gmail.com

Course Outline

Digital Logic Design

Course Contents:

Number Systems, Logic Gates, Boolean Algebra, Combination logic circuits and designs, Simplification Methods (K-Map, Quinn Mc-Cluskey method), Flip Flops and Latches, Asynchronous and Synchronous circuits, Counters, Shift Registers, Counters, Triggered devices & its types. Binary Arithmetic and Arithmetic Circuits, Memory Elements, State Machines. Introduction Programmable Logic Devices (CPLD, FPGA); Lab Assignments using tools such as Verilog HDL/VHDL, MultiSim


Reference Material:

1. Digital Fundamentals by Floyd, 11/e.
2. Fundamental of Digital Logic with Verilog Design, Stephen Brown, 2/e.





Logic Gates



- Not

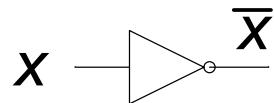

- And

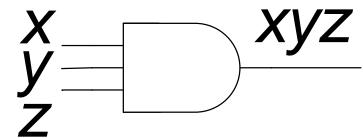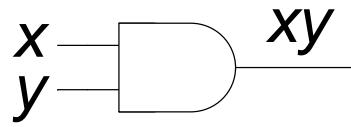

- Or

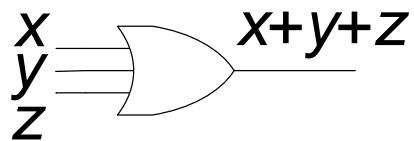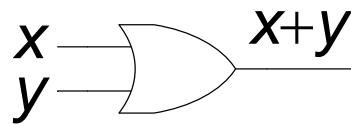


ArfanShahzadTech




WhatsApp-Contact Us
0345-5922495

Logic Gates cont


- Nand

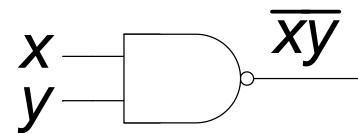

- Nor

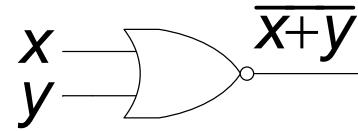

- Xor

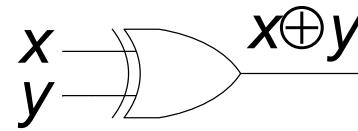

ArfanShahzadTech




WhatsApp-Contact Us
0345-5922495

Logic Gates cont

Conversion between circuits and equations

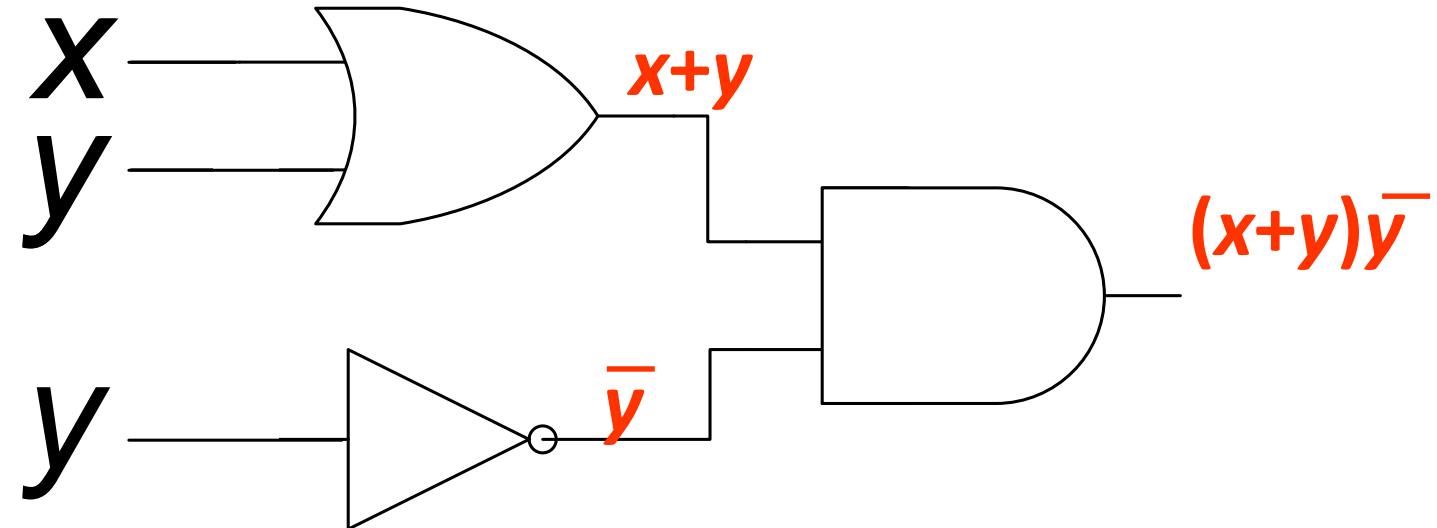- Find the output of the following circuit




- Answer: $(x+y)\bar{y}$ / Or $(x \vee y) \wedge \neg y$



Logic Gates cont

Conversion between circuits and equations

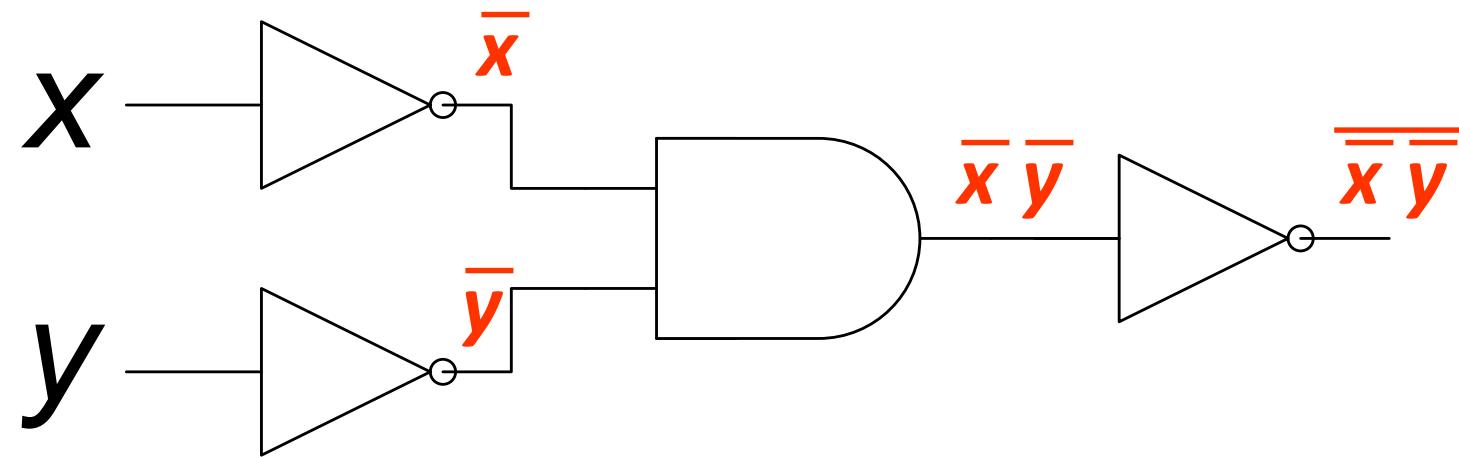- Find the output of the following circuit



Answer: $\bar{\bar{x}\bar{y}}$ /

Or $\neg(\neg x \wedge \neg y) \equiv x \vee y$



ArfanShahzadTech



WhatsApp-Contact Us
0345-5922495

Logic Gates cont

Conversion between circuits and equations

- Write the circuits for the following Boolean algebraic expressions
- $(\overline{x+y})x$

